

Temperature °Controls Pty Ltd

ACN: 075 298 592 ABN: 966 501 901 83



Sydney (Head Office): 7 Yamma St, Sefton, NSW 2162 Australia Ph: 61 2 9721 8644 Fax: 61 2 9738 9339

Melbourne: 8/280 Whitehall St, Yarraville VIC 3013 Australia Ph: 61 3 9687 0000 Fax: 61 3 9687 1900

Brisbane: 28a 121 – 125 Kerry Rd, Archerfield, QLD 4108 Australia Ph: 61 7 3373 8424 Fax: 61 7 3373 8067


W: www.temperature.com.au

E: sales@temperature.com.au



Inor Loop Isolator Application Notes

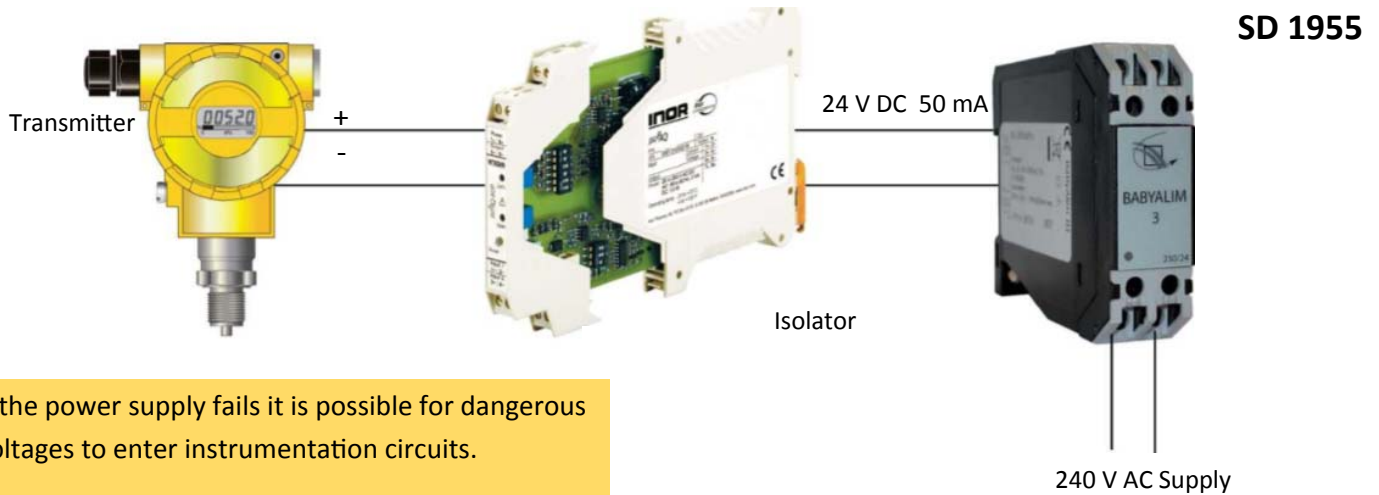
Prevent dangerous voltages from instrumentation circuits



If the power supply fails it is possible for dangerous voltages to enter instrumentation circuits.


The loop isolator will provide galvanic isolation of 1.5Kv 50Hz

Circuit Integrity

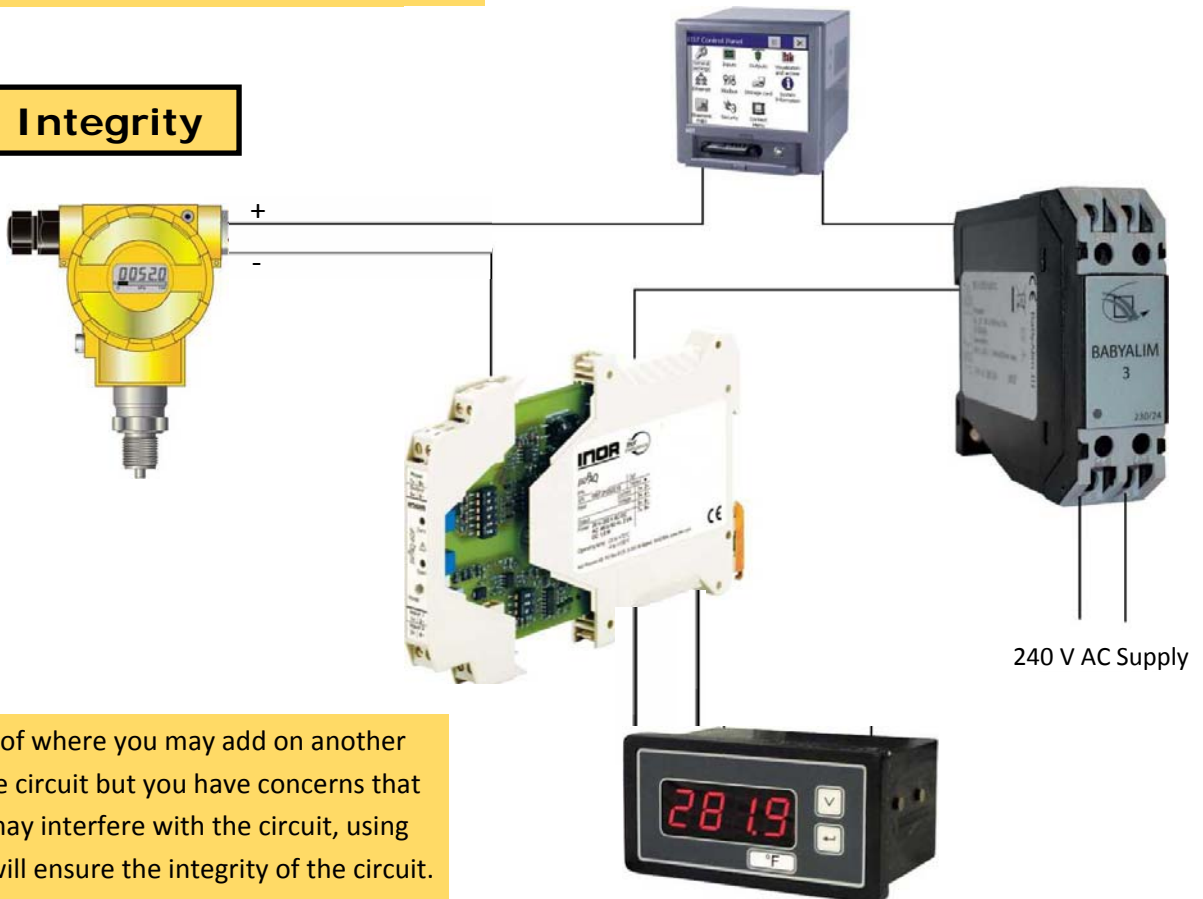


An example of where you may add on another device to the circuit but you have concerns that the device may interfere with the circuit, using an isolator will ensure the integrity of the circuit.

Common Voltage

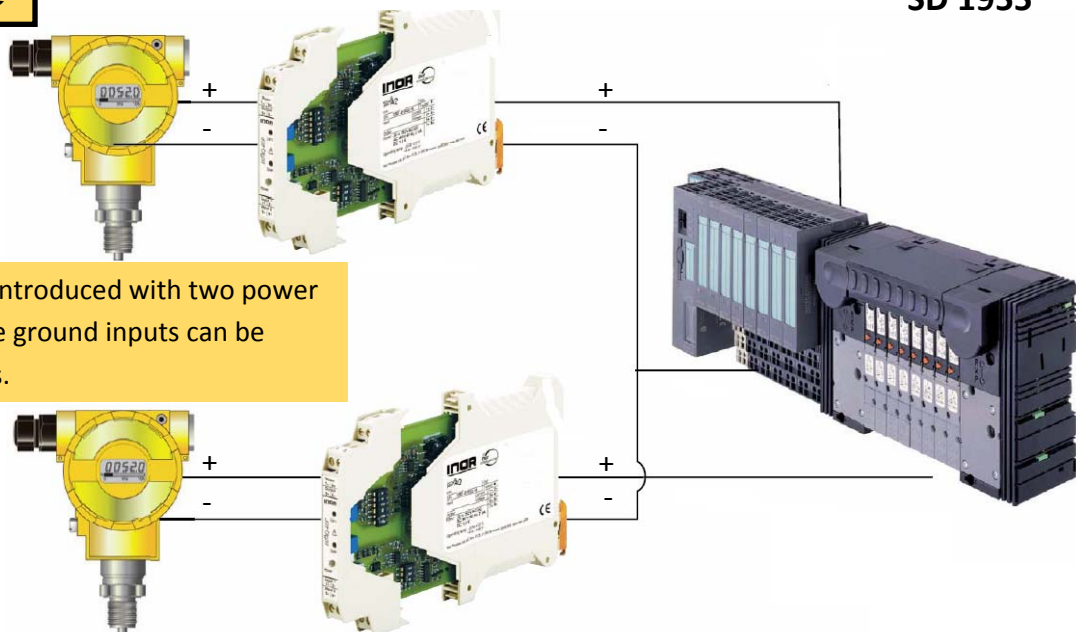


Eliminate errors that may be introduced with two power supplies. The common voltage ground inputs can be isolated from the transmitters.

Amplifying 4-20mA Loop

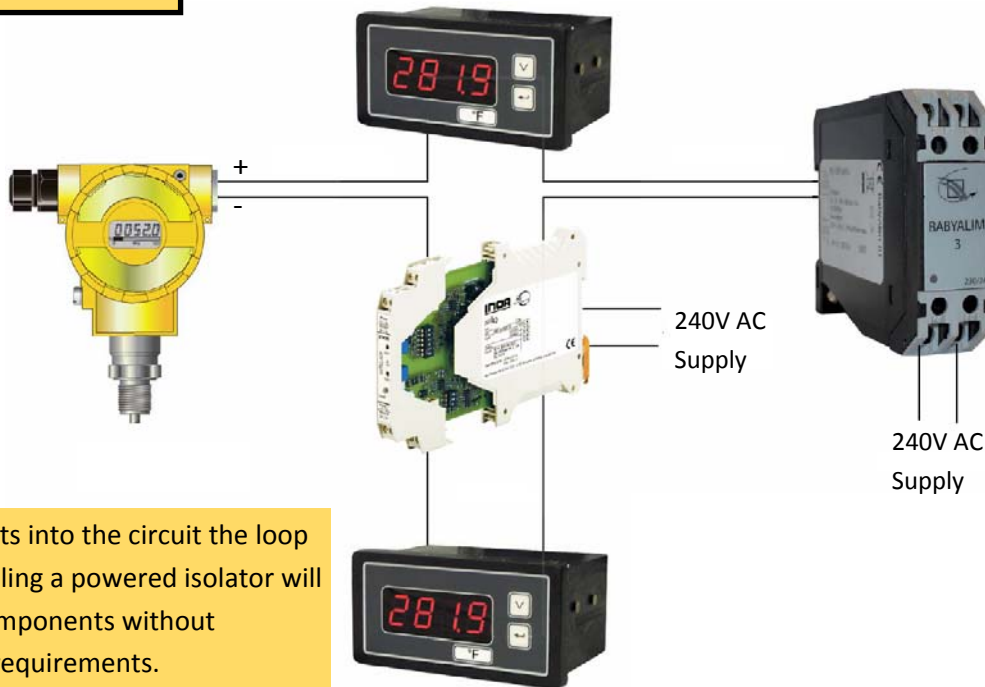

If you add too many components into the circuit the loop may become overloaded. Installing a powered isolator will allow you to integrate more components without concerns over the loop power requirements.

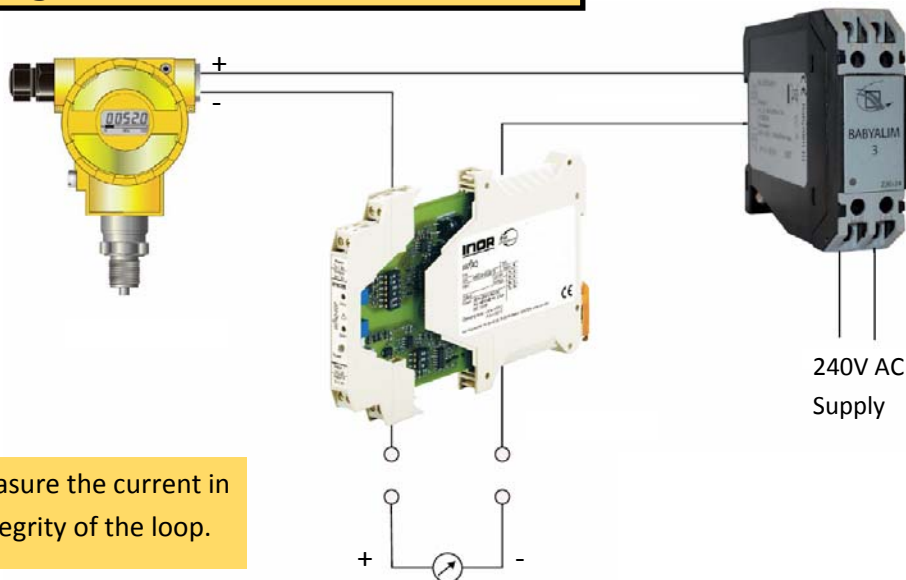Measure 4—20mA Signal and maintain circuit



An example of where you can measure the current in the loop with out breaking the integrity of the loop.